

16 BIT High Speed ComparatorAbdallah AboShoaib¹ and Malik Arqoup²¹1210211²1211686


ABSTRACT

Showing the theory of comparators and why we need them. Then , how to implement 16 bit one using 4 bits And demonstrate the steps of Digital designing and then schematic and layout for the fabrication process. Finally showing results and statistic .

1 | Theory And Workflow

Digital Desgin :

1- Bit Comparator :

 


1 1-bit comparator block diagram

$$A > B : A.B' , A = B : A'.B' + A . B$$


4- Bit Comparator :

 We can use the one bit to make the 4 one .



2 4bit comparator using 1 bit

16 – bit Comparator :

 


3 16 bit comparator using 4 bit

Schematic :


Using cmos technology and the roles of design aspects.

1-bit comparator :

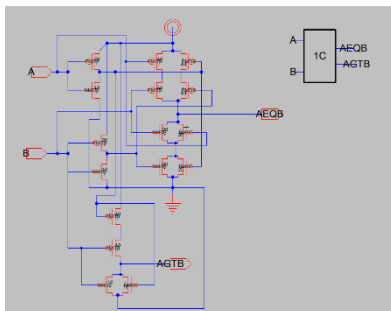


4 1bit Comparator cmos schematic

4 – bit Comparator :

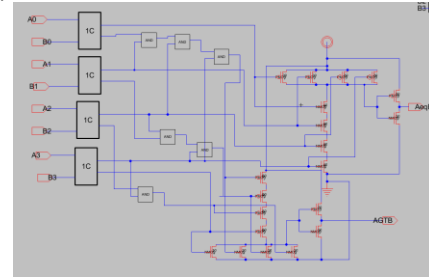

5 4bit comparator cmos schematic


16-bit comparator :

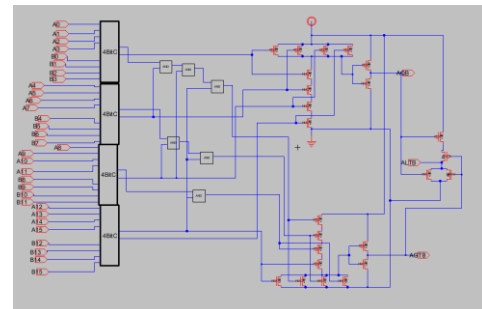

6 16- bit comparator cmos schematic


Layout :

1-bit :

 


7 1 bit Layout

4-bit:

 

8 4-bit Layout

16- bit :

 

Delay report :


```

vaeqb=7.08925e-009 FROM 1.74487e-007 TO 1.81576e-007
vaeqbt=7.06076e-009 FROM 3.80942e-007 TO 3.88003e-007
vagt看b=5.46814e-009 FROM 3.78905e-007 TO 3.84373e-007
vagt看bt=5.65048e-009 FROM 1.8459e-007 TO 1.90241e-007

```

4 bit :

schematic :

 

Delay and power report :

```

avg_power: AVG(i(vdd))=-2.30936e-007 FROM 0 TO 1e-006
peak_power: MAX(i(vdd))=-2.30935e-007 FROM 0 TO 1e-006


veqb=9.46711e-010 FROM 3.40423e-007 TO 3.4137e-007
veqbt=1.04156e-009 FROM 1.66971e-007 TO 1.68012e-007
vgtb=1.32564e-009 FROM 2.09545e-007 TO 2.10871e-007
vgb=6.97791e-010 FROM 7.60259e-007 TO 7.60956e-007

```

2 | Results and Statistic

1-bit comparator :

Schematic :

 


Delay report :

```


vaeqb=5.84739e-009 FROM 1.71227e-007 TO 1.77075e-007
vaeqbt=6.09705e-009 FROM 3.78882e-007 TO 3.84979e-007
vagt看b=8.36888e-009 FROM 3.56919e-007 TO 3.65288e-007
vagt看bt=5.46451e-009 FROM 1.87117e-007 TO 1.92582e-007

```

Layout :

 

Layout :

 

Delay report :


```

avg_power: AVG(i(vdd))=-7.92732e-006 FROM 0 TO 1e-006
peak_power: MAX(i(vdd))=8.44107e-006 FROM 0 TO 1e-006
veqb=1.07203e-009 FROM 3.50822e-007 TO 3.51894e-007
veqbt=1.53032e-009 FROM 1.73415e-007 TO 1.74946e-007
vgtb=1.81859e-009 FROM 3.80705e-007 TO 3.82524e-007
vgb=1.0047e-009 FROM 7.68181e-007 TO 7.69186e-007

```

16 – bit

schematic :

 

```
avg_power: AVG(1+(vdd))=-2.58342e-005 FROM 0 TO 1e-006
peak_power: MAX(1+(vdd))=8.23256e-005 FROM 0 TO 1e-006
vaeqb=3.21783e-009 FROM 1.53314e-007 TO 1.56532e-007
vaeqbt=4.71587e-009 FROM 1.21639e-007 TO 1.26355e-007
vaeqb=3.99212e-009 FROM 1.41111e-007 TO 1.45103e-007
vaeqb=5.27217e-009 FROM 3.76839e-007 TO 3.82111e-007
vlth=3.19297e-009 FROM 2.86701e-007 TO 2.89894e-007
vltht=3.28306e-009 FROM 1.57499e-007 TO 1.60782e-007
```

Timing diagram for the 74163 4-bit binary counter. The diagram shows five signals over 10 clock cycles. 'clock' is a periodic square wave. 'enA' is a pulse at the start. 'enB' is a pulse at the start. 'enC' is a pulse at the start. 'enD' is a pulse at the start. 'enE' is a pulse at the start. The counter output 'Q' is shown in four bits: Q3 (blue), Q2 (green), Q1 (yellow), and Q0 (purple). The counter starts at 0000 and counts up to 1011 (decimal 11) before wrapping back to 0000.

```
avg_power: AVG(i(vdd))=-2.77042e-005 FROM 0 TO 1e-006
peak_power: MAX(i(vdd))=7.57739e-005 FROM 0 TO 1e-006
vaeqb=3.073e-009 FROM 1.59403e-007 TO 1.62476e-007
vaeqbt=4.04751e-009 FROM 1.30442e-007 TO 1.34489e-007
vagb=5.85466e-009 FROM 1.87503e-007 TO 1.93357e-007
vagt=5.08886e-009 FROM 3.14594e-007 TO 3.19683e-007
vlbt=3.941e-009 FROM 2.92957e-007 TO 2.96898e-007
vlbtb=3.70259e-009 FROM 1.92886e-007 TO 1.96589e-007
```

1-bit : 0.04572 μm^2

5

